



VLSI PROJECT REPORT


Name : Vinkesh Bansal

Roll No. : 2021102020

NGSPICE

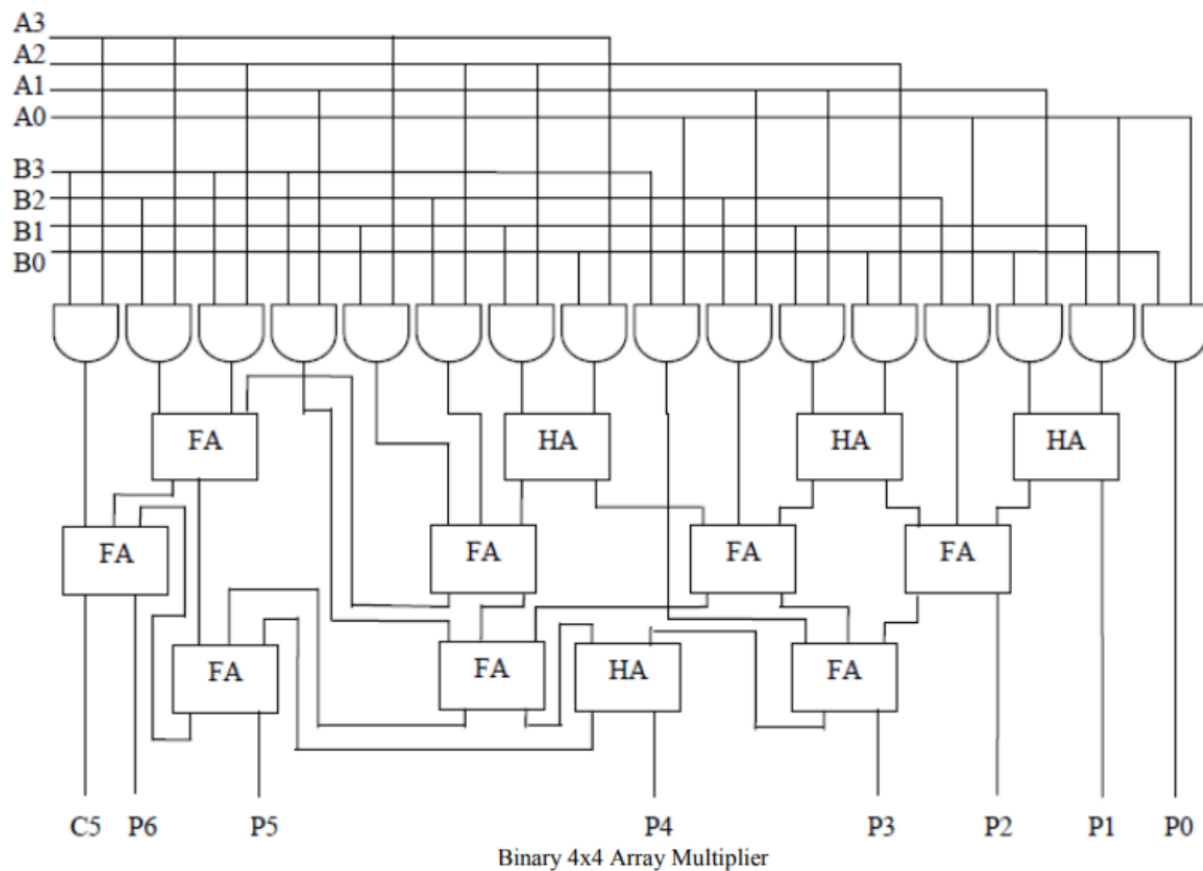1)

To make a ngspice circuit i used the following circuit:



i made a subckt for fulladder and a and gates using pmos and nmos gates and used them to implement the above circuit

```
subckt adder nodeA nodeB nodeC nodesum nodecarry vddd! gndd!
Mn1 node11 nodeA gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn2 node10 nodeA gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn3 node10 nodeB gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn4 node9 nodeC gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn5 node9 nodeA gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn6 node9 nodeB gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn7 node8 nodeA gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn8 node7 nodeB node8 gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn9 node6 nodeC node7 gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn10 node6 node12 node9 gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn11 node12 nodeC node10 gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn12 node12 nodeB node11 gndd! nmos W={1*XX*Wmin} L={Lmin}
Mp1 node1 nodeA vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp2 node2 nodeA vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp3 node2 nodeB vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp4 node3 nodeC vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp5 node3 nodeA vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp6 node3 nodeB vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp7 node4 nodeA vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp8 node5 nodeB node4 vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp9 node6 nodeC node5 vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp10 node6 node12 node3 vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp11 node12 nodeC node2 vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp12 node12 nodeB node1 vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp13 nodesum node6 vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp14 nodecarry node12 vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mn13 nodesum node6 gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn14 nodecarry node12 gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}

.ends adder


.subckt and nodeA nodeB node6 vddd! gndd!
Mp1 node5 nodeA vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mp2 node5 nodeB vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
Mn1 node4 nodeA gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn2 node5 nodeB node4 gndd! nmos W={1*XX*Wmin} L={Lmin}
Mn3 node6 node5 gndd! gndd! nmos W={1*XX*Wmin} L={Lmin}
Mp3 node6 node5 vddd! vddd! pmos W={2*XX*Wmin} L={Lmin}
.ends and
```

i gave a input which takes into account every possible combination

```
VinA0 nodeA0 0 pulse 0 1 0 100p 100p 50n 100n
VinA1 nodeA1 0 pulse 0 1 0 100p 100p 100n 200n
VinA2 nodeA2 0 pulse 0 1 0 100p 100p 200n 400n
VinA3 nodeA3 0 pulse 0 1 0 100p 100p 400n 800n
VinB0 nodeB0 0 pulse 0 1 0 100p 100p 800n 1600n
VinB1 nodeB1 0 pulse 0 1 0 100p 100p 1600n 3200n
```

```
VinB2 nodeB2 0 pulse 0 1 0 100p 100p 3200n 6400n
VinB3 nodeB3 0 pulse 0 1 0 100p 100p 6400n 12800n
```

the plot of the following is:

 

2)

Now to calculate power of the circuit i wrote a python script which gives every input to my spice file

i calculated power by multiplying current and voltage of every input

```
power = inA3*iinA3 + inB3*iinB3 + inA2*iinA2 + inB2*iinB2 + inA1*iinA1 + inB1*iinB1 + inA0*iinA0 + inB0*iinB0
```

i stored every power in the file `power_smamples.txt` i got the maximum power as:

```
max leakage power: 5.72481E-07
```

3)

To calculate delay i found 50 paths in the circuit and i put in a file `delay.txt`

Max delay came out to be:


```
max delay :      -4.246739e-09
```

VERILOG

i wrote structural code for the following :

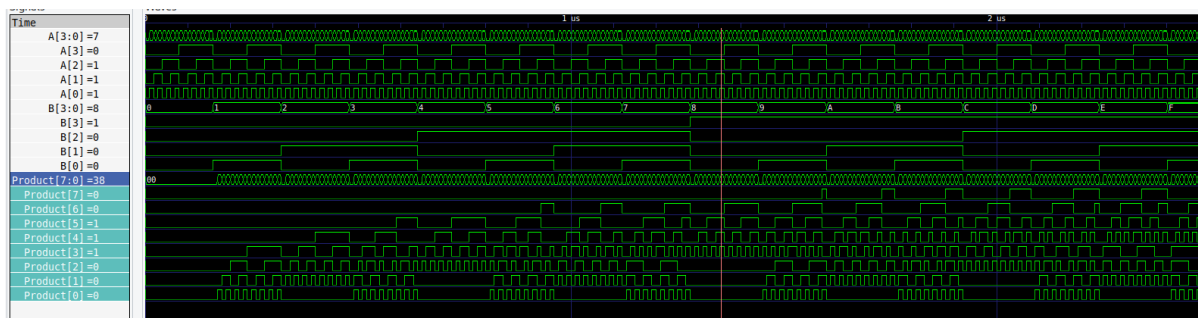1. Half Adder
2. Full adder
3. 4 bit adder
4. Multiplier


then i wrote a test bench code to give all inputs to my file and my output(gtkwave) was:



In this we can also see that 7 multiplied by 8 is 56

and output coming is in hexadecimal which is 38 = $3 \times 16 + 8 = 56$ in binary which is correct

this design is :

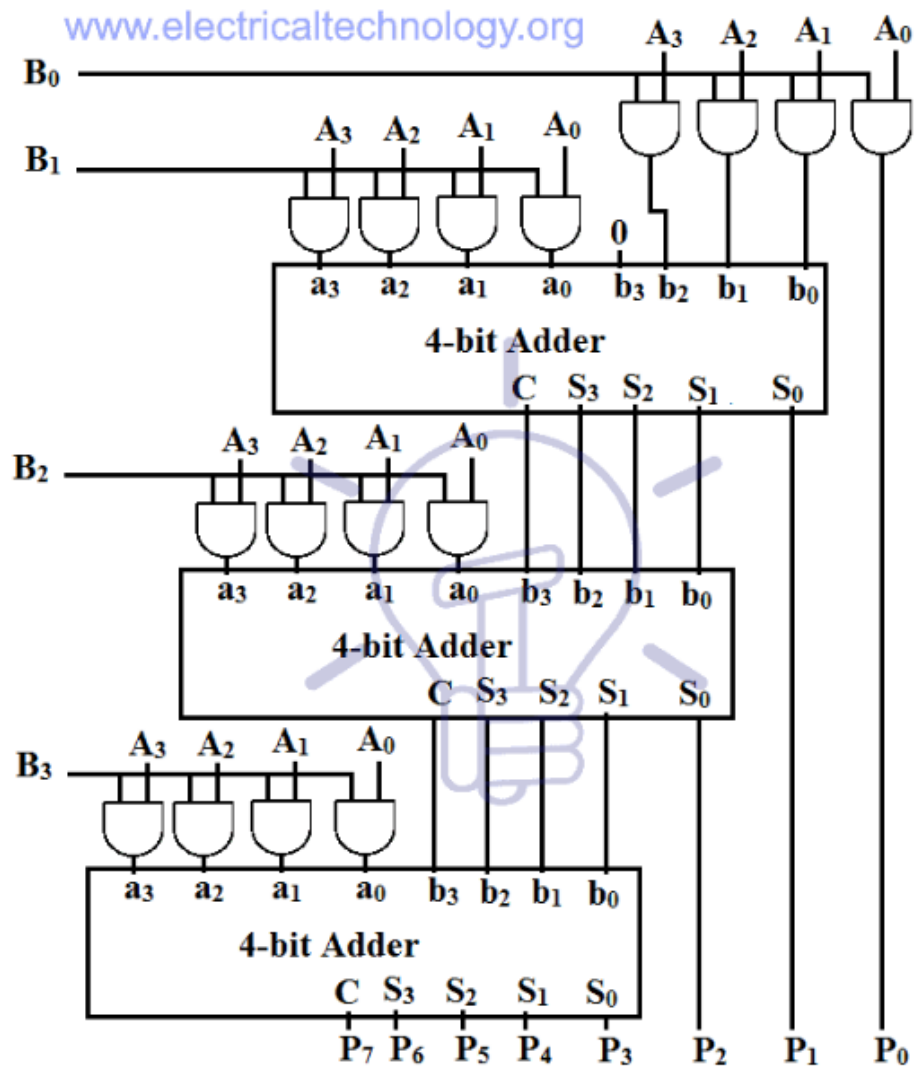


now we can verify the output of 2 circuit and verify their functioning

MAGIC

i made my magic layout using different blocks from start like invert, and gate, or gate, adder, xor and then used all of them in the final layout

my layout is:

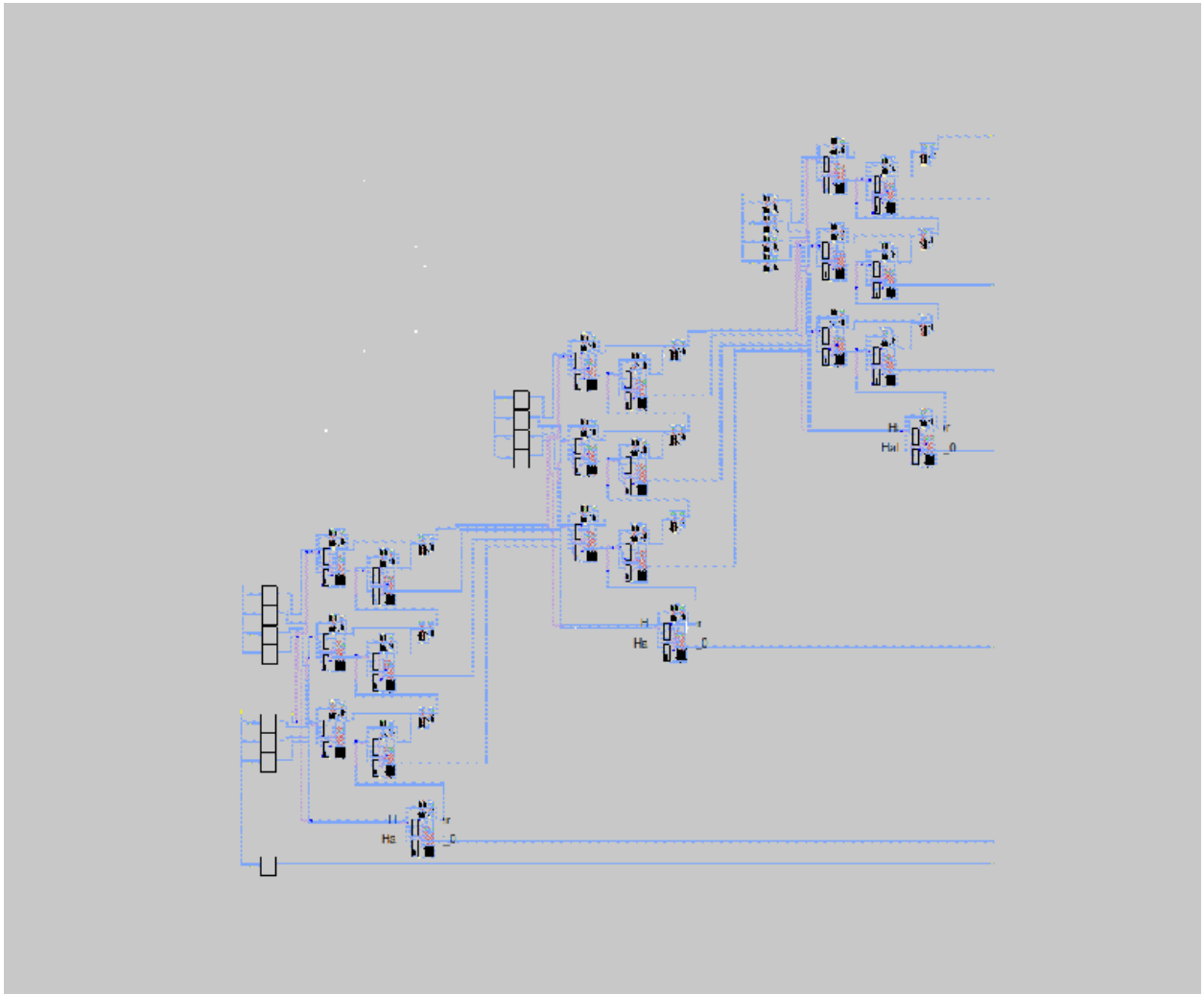

extract it into spice by the following commands:

```
extraxt all  
ext2spice Multiplier_4x4.ext
```

then in the spice code change nfet to nmos and pfet to pmos,give inputs and plotted the output and verified that it is working